

## QUESTION 1

- (a) State two Kirchhoff's Law. Define **ONE (1)** of them by sketching an appropriate diagram to support the answer. (5 marks)
- (b) Based on the Figure 9, calculate the current flow through the  $4\Omega$  resistor using **mesh analysis**. (10 marks)

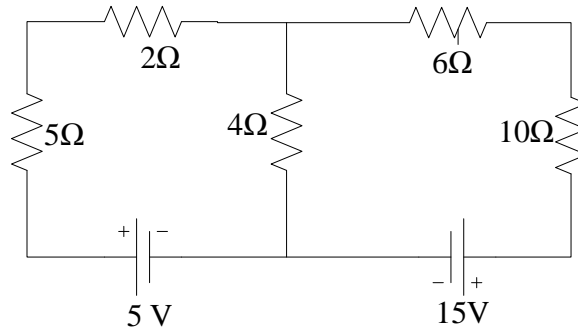


Figure 9

- (c) For the Figure 10 below, calculate  $I_{RL}$  using Thevenin's Theorem. (10 marks)

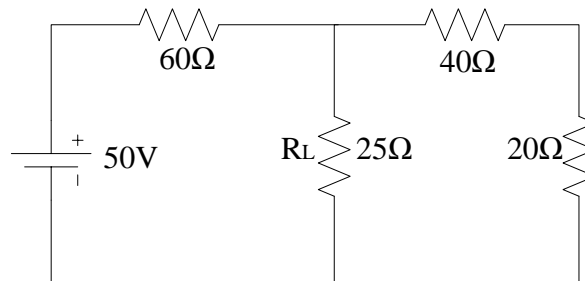


Figure 10

## QUESTION 2

- a. Based on Figure C (2a), calculate the current flow through  $15\Omega$  resistor using Kirchhoff's Law.

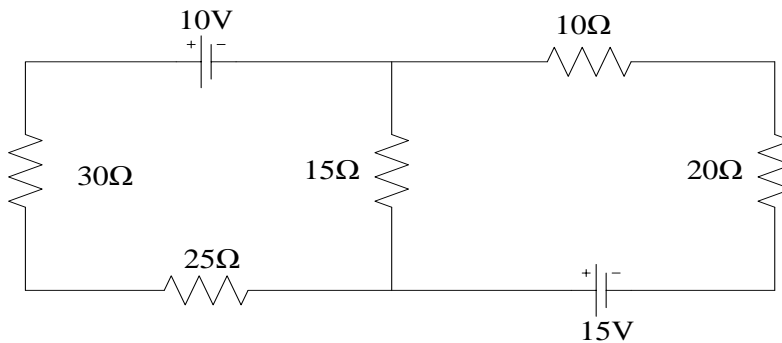


Figure C (2a)

(15marks)

- b. Based on Figure C (2b), calculate :
- Total resistance
  - Total current
  - Current flow through  $10\Omega$  resistor
  - Voltage drop at  $15\Omega$  resistor

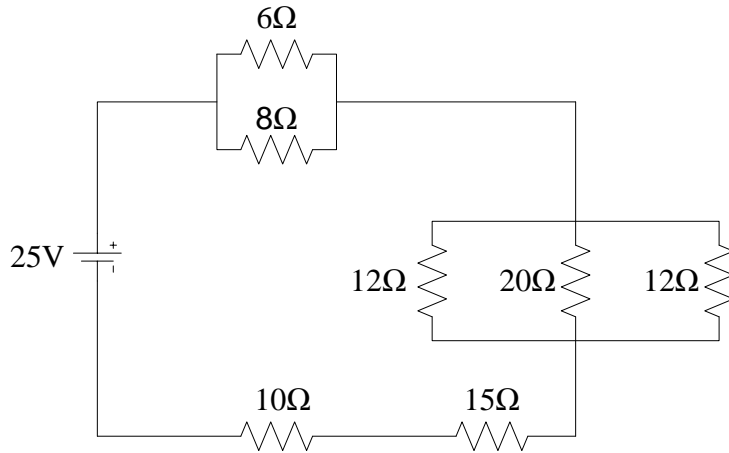


Figure C (2b)

(10marks)

### QUESTION 3

- (a) Sketch the graph Voltage in volt versus Current in ampere. What is the quantity that will be represented by the slope of the graph? (3 marks)
- (b) For the Figure 11 below, calculate :

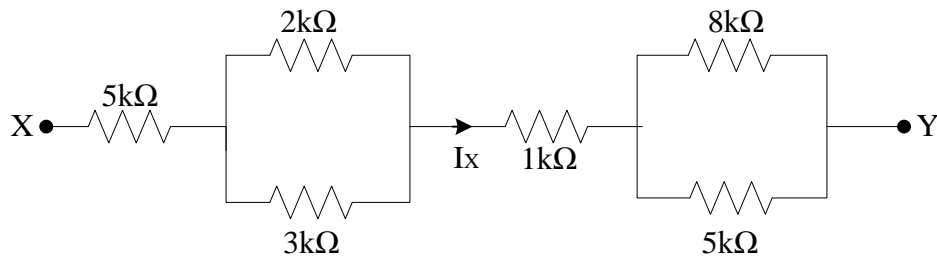


Figure 11

- Equivalent resistance at terminal XY (3 marks)
- Voltage across  $2k\Omega$  resistor if the voltage terminal XY is 150V. (3 marks)
- Current through  $5k\Omega$  resistor if  $I_x = 20\text{mA}$ . (3 marks)

- (c) Based on the Figure 12, using Delta-Star Transformation, calculate the current flow and voltage drops at  $15\Omega$  resistor. (13 marks)

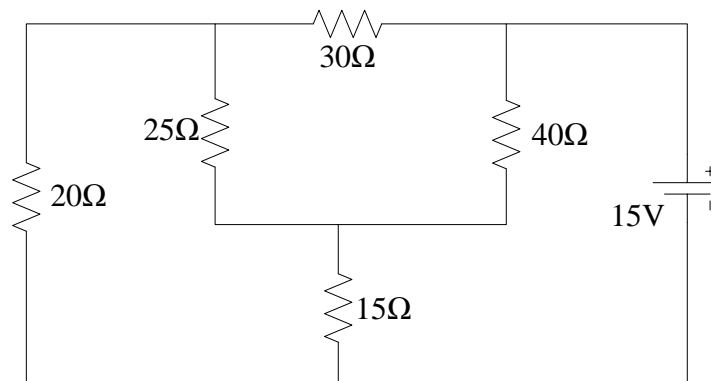


Figure 12

#### QUESTION 4

- a. Using the Thevenin Theorem find the  $R_L=5\Omega$  in Figure C(1a)


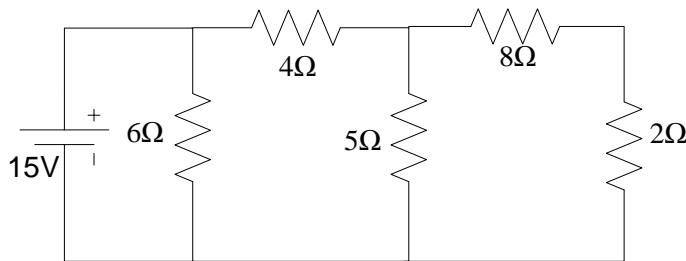


Figure C(1a)

(15 marks)

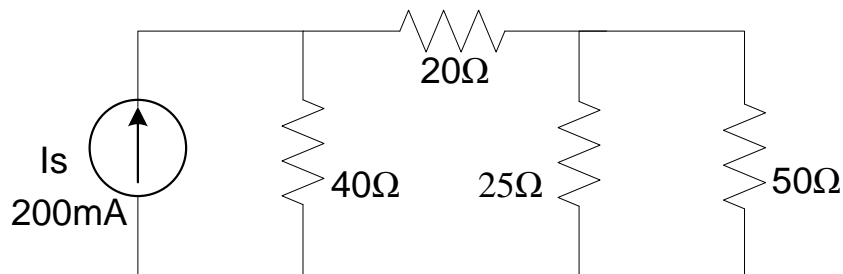
- b. Using the Norton Theorem find the current flow through  $R_L= 25\Omega$ .



(10 marks)

### QUESTION 5

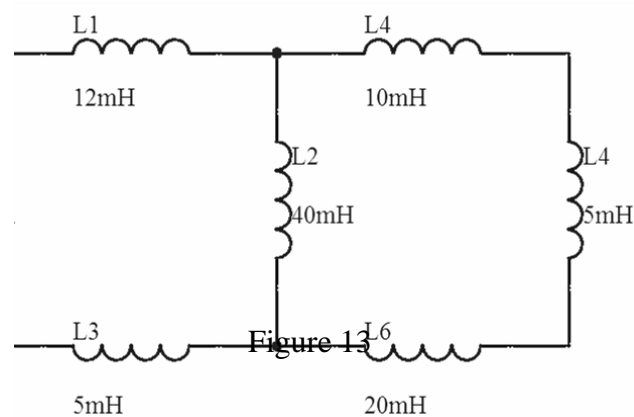- (a) Briefly explain Faraday's Law. (3 marks)
- (b) The current 3A is flowing in a solenoid with 200 turns and 25mm length. Given that the solenoid diameter is 10mm,  $\mu_r$  is 650 and  $\mu_0$  is  $1.256 \times 10^{-6}$ . Find the value of inductance that exists in the solenoid. (5 marks)
- (c) A circuit has a  $25\Omega$  resistor that is connected in series with a 1.5H inductor. The circuit is connected to 200V power supply. Determine the:
- Time constant (2 marks)
  - Current in time (i) (4 marks)
  - Current at 0.02s (2 marks)
  - Initial rate of rising current (2 marks)
  - Energy stored in inductor (2 marks)
- (d) Based on the Figure 13, find the total inductance and energy stored in the circuit. (5 marks)



### QUESTION 6

- a. Based on Figure C (2a), calculate the total inductance at terminal A B.

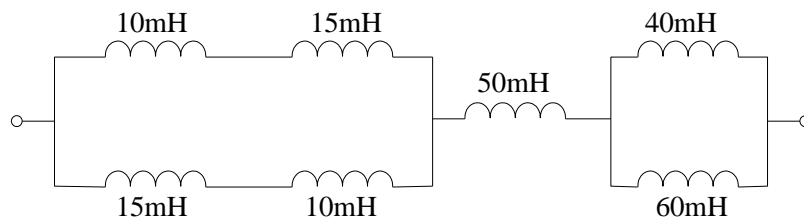


Figure C (2a)

(4 marks)

- b. If the total capacitance of the two  $25\mu\text{F}$  capacitor connected in series and the value of one capacitor is  $40\mu\text{F}$ . Draw the circuit and calculate the value of other capacitor. (5 marks)
- c. A resistance of  $15\text{k}\Omega$  connected in series with inductance of  $25\text{H}$  across dc supply of  $150\text{V}$  power supply. Find :
- Time constant
  - Maximum current
  - Time taken for current to rise at  $0.02\text{A}$ .
  - Energy stored
  - Sketch a labeled graph to show the rising current. (12 marks)
- d. A coil 250 turns is wound to an iron core with cross sectional area  $5\text{cm}^2$  and  $20\text{cm}$  length. If relative permeability is 750 and current  $5\text{A}$  flow through it, calculate the coil inductance. (4 marks)

### QUESTION 7

- a. Based on the Figure C (1b), calculate the total inductance.

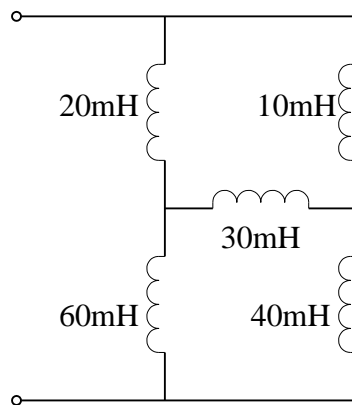


Figure C (1b)

(6 marks)

- b. A capacitor plate has  $1\text{mm}$  length and  $0.2\text{mm}$  width and separate by  $0.05\text{mm}$  dielectric. If relative permittivity of dielectric is 450. Calculate the capacitance. ( $\epsilon_0 = 8.854 \times 10^{-12}$ ) (5 marks)
- c. An  $150\mu\text{F}$  capacitor connected in series with  $1.5\text{k}\Omega$  resistor connected across a  $220\text{V}$  DC supply. Calculate :
- Initial value of current
  - Time constant
  - Equation of current in time function
  - Value of current at time equal to (ii)
  - Rate at which current begins to decrease. (14 marks)