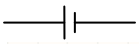
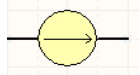

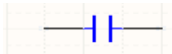






1. The Coulomb is the unit of
 A. Power
 B. Voltage
 C. Energy
 D. Charge
2. These units are the SI unit **EXCEPT** :
 A. Mass
 B. Length
 C. Electric Current
 D. Voltage
3. The/an will be required between two points for current to flow in a circuit.
 A. Energy
 B. Power
 C. Potential difference
 D. Resistor
4. The voltage is a unit of
 A. Current
 B. Power
 C. Energy
 D. Electromotive force
5. Which of the following is TRUE :
 A.  Battery
 B.  Voltmeter
 C.  Variable resistor
 D.  Resistor
6. Which of the following circuit diagram symbol is **FALSE**?
 A. Switch 
 B. Fuse 
 C. Inductor 
 D. Cell 
7. Quantity of electricity or charge could be stated as:
 A. $Q = Pt$
 B. $Q = It$
 C. $Q = Wt$
 D. $Q = Et$
8. The quantity of electricity is Q ,
 A. $Q = it$
 B. $Q = iR$
 C. $Q = iG$
 D. $Q = i^2t$
9. Potential difference is needed to flow the _____ in the circuit.
 A. Power
 B. Energy
 C. Resistance
 D. Current

10. 45 μ s is equivalent to:

- A. 0.045
- B. 45 minutes
- C. 0.000045s
- D. 0.45s

11. Which statements TRUE about primary and secondary cell?

- i. Primary cell cannot be recharged
 - ii. Secondary cell can be use once
 - iii. Secondary cell is reversible
- A. i and ii
 - B. i and iii
 - C. ii and iii
 - D. All of the above

12. Which statement is **TRUE** about primary and secondary cell:

- A. Primary cell is disposable and secondary cell is rechargeable.
- B. Primary cell is expensive and secondary cell is cheap.
- C. Primary cell is a wet cell and secondary cell is a dry cell.
- D. Primary cell has high power level discharge and secondary cell has low power discharge.


13. A battery consist of :

- A. A cell
- B. A number of cell
- C. A generator
- D. A circuit

14. How many cell is needed to produce 9V if e.m.f each cell is 1.5V

- A. 8 cells in series
- B. 6 cells in parallel
- C. 8 cells in parallel
- D. 6 cells in series

15. Which of the following electrical component symbol is voltmeter?

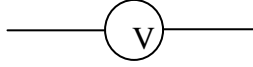- A. 
- B. 
- C. 
- D. 

16. How long must the current of 50mA flow so that the charge of 40C can be transferred?

- A. 60s
- B. 800s
- C. 100s
- D. 6 minute

17. The power dissipated by the resistor of 4 Ω when the current of 5A passes through is:

- A. 6.25W
- B. 20W
- C. 80W
- D. 100W

18. Which statement is TRUE

- A. Resistance is directly proportional to the cross sectional area.
- B. Resistance is inversely proportional to the resistivity.
- C. Resistance is directly proportional to the length.
- D. Resistance is inversely proportional to the length.

19. Given resistivity = $1.83 \times 10^{-8} \Omega\text{m}$, length = 100m and $A = 1.5 \times 10^{-6} \text{ m}^2$. What is the value of resistance?

- A. 12.2 Ω
- B. 1.22 Ω
- C. 122 Ω
- D. 1.2 k Ω

20. Resistance is $R = \frac{\rho l}{A}$, where ρ is:

- A. Cross sectional area
- B. Resistivity
- C. Current
- D. Length

21. Electrical resistance depends on the following factors, **EXCEPT**:

- A. Length of conductor
- B. Temperature
- C. Cross sectional area of conductor
- D. Shape of the conductor

22. If voltage in a circuit 12V and the total resistance is 6 Ω , what is the current flow?

- A. 2A
- B. 3A
- C. 4A
- D. 2.5A

23. The potential difference will be applied to a 1k Ω resistance in order that the current of 100 μA may flow is:

- A. 1V
- B. 100V
- C. 0.1V
- D. 10V

24. If two 4 Ω resistors were connected in series, the effective resistance of the circuit is:

- A. 2 Ω
- B. 4 Ω
- C. 8 Ω
- D. 10 Ω

25. The following are the effects of an electric current **EXCEPT**

- A. Heating effect
- B. Chemical effect
- C. Magnetic effect
- D. Temperature effect

26. Potential difference is the quantity need to _____.

- A. Drop the voltage at the resistor
- B. Flow the current in circuit
- C. Dissipate the power of circuit
- D. Resist the current in the circuit

27. A 150W electric light bulb is connected to a 200V supply. Determine the current flowing in the bulb.

- A. 0.3A
- B. 0.5A
- C. 0.75A
- D. 0.125A

28. Which is the effect of an electric current?

- A. Resistant effect
- B. Pole effect
- C. Shape effect
- D. Magnetic effect

29. The current flowing in the branches of a d.c circuit may be determined using:
- | | |
|------------------|-----------------------------|
| A. Lenz's law | C. Kirchoff's laws |
| B. Faraday's law | D. Fleming's left-hand rule |

30. All the following statements are true, **EXCEPT**

- | |
|--|
| A. I_{TH} is the ratio of source voltage and Thevenin resistance |
| B. Thevenin voltage is the open circuit voltage at the required terminals |
| C. R_{TH} is the total resistance seen at required terminals by replacing short circuit at voltage sources |
| D. Thevenin equivalent circuit consist of Thevenin resistance, load resistance and single voltage source in series |

31. Which statement is **FALSE** in maximum power transfer?

- | | |
|-------------------|-------------------------------------|
| A. $V_S = E$ | C. $I_L = I_{\text{short circuit}}$ |
| B. $R_L = R_{IN}$ | D. Efficiency = 100% |

32. The total resistance of the circuit in Figure A(9) is

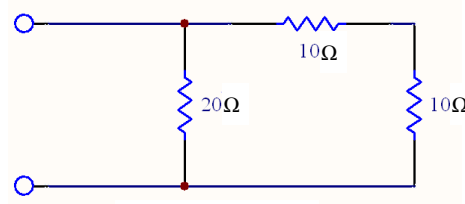


Figure A (9)

- | | |
|--------|--------|
| A. 30Ω | C. 10Ω |
| B. 20Ω | D. 5Ω |

33. How much the energy consumed if the 250Watt power is transferred in 2 minutes.

- | | |
|----------|----------|
| A. 30 kJ | C. 40 kJ |
| B. 35 kJ | D. 45 kJ |

34. The main effect of electric current and applications are true, **EXCEPT** :

- | | |
|-----------------------------------|--------------------------------|
| A. Chemical effect - electrolysis | C. Heat effect – filament bulb |
| B. Resistance effect – resistor | D. Magnetic effect – inductor |


35. Determine the voltage which be applied to a 3kΩ resistor such that the current of 6mA may flow.

- | | |
|-------|--------|
| A. 2V | C. 18V |
| B. 5V | D. 20V |

36. 'In the complete circuit, the sum of the voltage drop for each resistor is equal to the terminal voltage'. This statement is referred to :

- | | |
|------------------------|---------------------------|
| A. Voltage Divide Rule | C. Kirchoff's Current Law |
| B. Current Divide Rule | D. Kirchoff's Voltage Law |

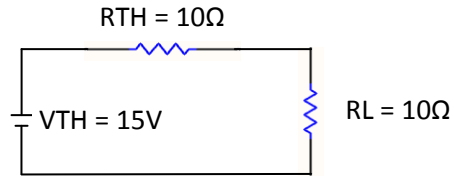37. Based on the Figure A(13) find I_{TH}



- | | |
|-----------|-----------|
| A. 0.15 A | C. 0.55 A |
| B. 0.35 A | D. 0.75 A |

38. Which of the following statements is TRUE?

- A. V_{TH} is the short circuit voltage at the required terminal
- B. I_{TH} is the ratio of source voltage, Thevenin resistance and load resistance
- C. I_{TH} is a total resistance seen at required terminal by open circuit at voltage source
- D. Thevenin equivalent circuit consists of single resistance and single voltage source in series

39. The following factors that effect capacitance EXCEPT

- | | |
|----------------------------|--------------------------------|
| A. Surface area of plate | C. Material between two plates |
| B. Thickness of dielectric | D. Length between two plates |

40. The base unit of capacitance is _____.

- | | |
|----------|------------|
| A. Henry | C. Farad |
| B. Ohm | D. Siemens |

41. If four capacitors are connected in **PARALLEL**, formulate the total capacitance :

- A. $C_T = C_1 + C_2 + C_3 + C_4$
- B. $C_T = \frac{1}{C_1 + C_2 + C_3 + C_4}$
- C. $C_T = C_1 \times C_2 \times C_3 \times C_4$
- D. $C_T = \frac{C_1 \times C_2}{C_3 \times C_4}$

42. Which types of capacitor below is unpolarised capacitor?

- | | |
|--------------|----------------------|
| i. Mica | iii. Air-gap |
| ii. Ceramic | iv. Electrolytic |
| A. i and ii | C. i, ii and iii |
| B. ii and iv | D. i, ii, iii and iv |

43. Four $2\mu\text{F}$ capacitors are connected in parallel. The equivalent capacitance is

- | | |
|---------------------|------------|
| A. $0.5\mu\text{F}$ | C. 8μ |
| B. $2\mu\text{F}$ | D. 10μ |

44. Which of the following statement is **FALSE**.
The capacitance of capacitor
- A. depends on the number of plates
 - B. is proportional to the distance between the plates
 - C. is proportional to the cross-sectional area of the plates
 - D. is proportional to the relative permittivity of the dielectric
45. 'The induced e.m.f is the product of self-inductance and the rate of change in current.'
Which formula is related to this statement?

- A. $e = -N \frac{d\phi}{dt}$
- B. $e = L \frac{di}{dt}$
- C. $e = -M \frac{di}{dt}$
- D. $e = L \frac{d\phi}{dt}$

46. The following factors influence the inductors, EXCEPT
- A. Number of turns in a coil
 - B. Diameter circumference
 - C. Type of core
 - D. Dielectric material
47. Formulate the total inductance L_T in Figure 1.

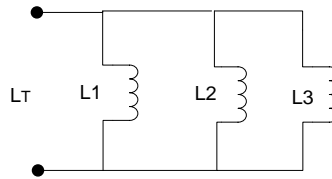


Figure 1

- A. $L_T = L1 + L2 + L3$
 - B. $L_T = \frac{1}{L1} + \frac{1}{L2} + \frac{1}{L3}$
 - C. $L_T = \frac{L1 \times L2 \times L3}{L1 + L2 + L3}$
 - D. $\frac{1}{L_T} = \frac{1}{L1} + \frac{1}{L2} + \frac{1}{L3}$
48. The following statements are true about characteristics of magnetic field EXCEPT
- A. Forming a closing loop
 - B. Has a certain direction
 - C. Repel between one another
 - D. Crossed against each other
49. Which is the rule to determine the magnetic field direction.
- A. Len's Rule
 - B. Magnetic Rule
 - C. Left Hand Rule
 - D. Screw Rule
50. Electromagnetism is defined as follows, EXCEPT
- A. Magnetism caused by a permanent magnet
 - B. Magnetism produced by an electric current
 - C. Magnetism produced by electric charge in motion
 - D. Transient magnetism of conductor caused by electric current.

51.

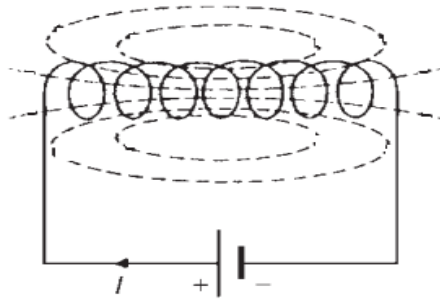


Figure 2

The Figure 2 shows the magnetic field produced by solenoid and it seen to be similar to a bar magnet. Based on Figure 2, what polarity the magnetic field produce?

- | | |
|-------------------|-------------------|
| A. South to East | C. North to South |
| B. South to North | D. North to West |

52. “The ratio between the potential difference or voltage and the thickness of dielectric.”

The statement above is the definition of

- | | |
|--------------------------|----------------------------|
| A. Electric flux | B. Electric field strength |
| A. Electric flux density | C. Absolute permittivity |